



Advanced Computer Organization II

Advanced Computer Architecture II

Introduction to Verilog HDL



Reference

- D. E. Thomas and P. R. Moorby: The Verilog Hardware Description Language, Kluwer Academic Pub., 1995.

Why do we use HDL?

■ History of design methodology

- 1980's: 10kTr./chip (\doteq 2.5k NAND2/chip)

- Gate level design (schematic entry)

- 1990's: 1,MTr./chip (\doteq 250k NAND2/chip)

- Register Transfer Level (RTL) design

(Hardware Description Language)



- 2000's~: over 100MTr./chip
(\doteq 25M NAND2/chip)

- System level design

- Platform based design

- IP based Design (IP reuse)

  - High level synthesis (Behavioral design, C like language)





Why Hardware Description Language?

- Standardized HDL
 - Used for digital circuit design in world wide
 - Verilog HDL: Gateway design from 1984, IEEE Standard 1364
 - VHDL: DARPA (Defense Advanced Research Projects Agency, USA) from 1981, IEEE Standard 1076
- Support many design methodology and technology
 - Wired Logic vs. Microprogram Machine, ...
- Independent from device technology and process
 - e.g. CMOS, TTL, ECL, ...
- Widely description level
 - Architecture, Behavior, register transfer and gate level
- Support large scale design and design re-use
 - Library, IP (Intellectual Property)




What is Verilog HDL?

- Verilog = Verify + Logic (coined word)
- History
 - Developed as description language for logic simulator by Gateway Design Inc. in 1984
 - Followed by CADENCE Inc.
 - OVI (Open Verilog International)
<http://www.ovi.org/>
 - Standardized
 - IEEE Standard 1364-1995,2001,2005
 - IEEE Standard 1800-2005,2009,2012 (System Verilog)


Features of Verilog HDL

- Widely description level


- Architecture Level

 


- Behavior Level

 


- Register Transfer Level

 

- Gate Level

 

SoC design & implementation flow

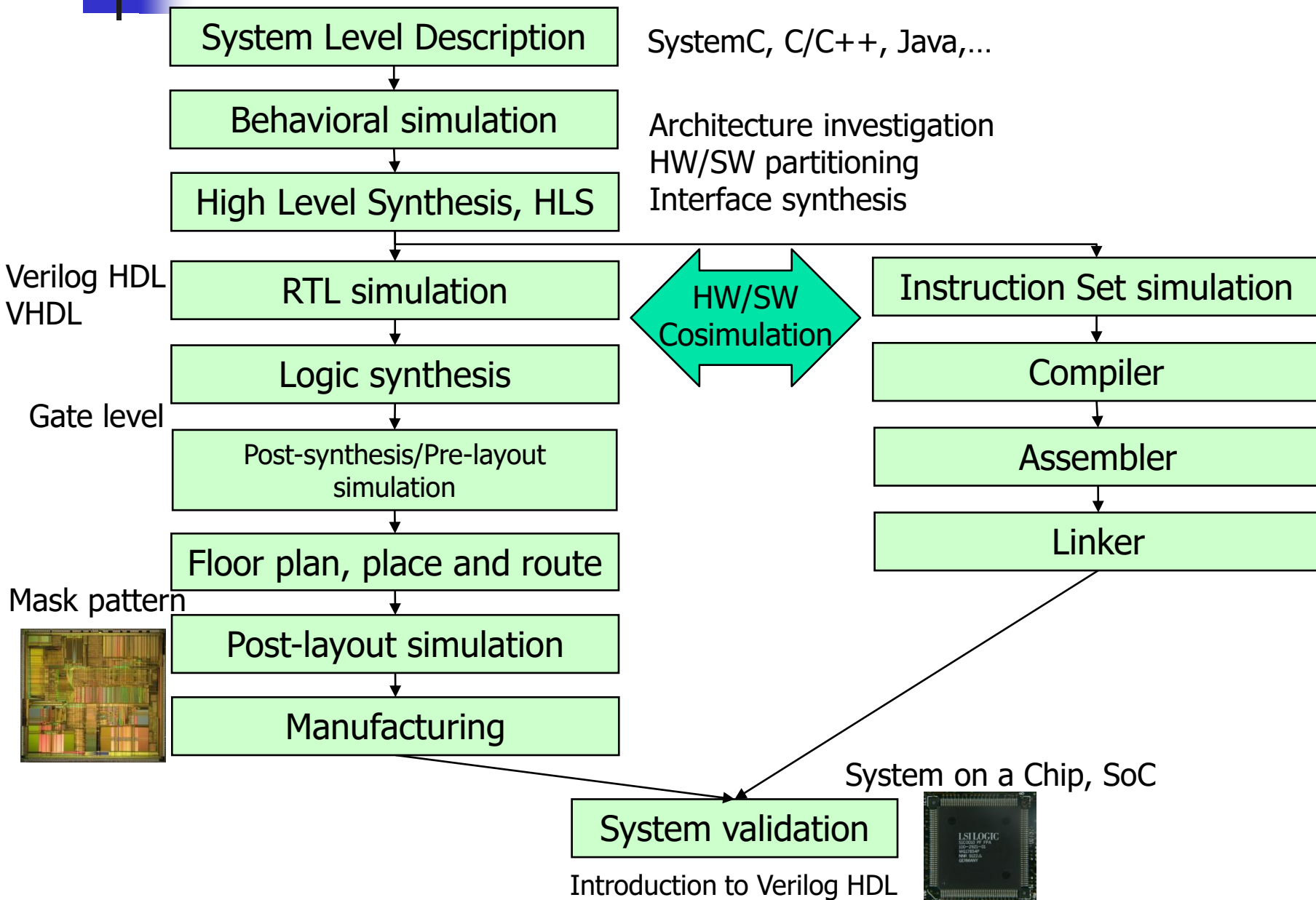




Introduction to Verilog HDL

Gate Level Description

Examples: Half adder and Full adder


Half Adder (Gate Level)

 

Symbol

Truth Table

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

Logic Circuit

```
module description
module
...
endmodule
```

Module name (commonly same as file name)

```
module halfadder ( A, B, S, C );
  input  A, B;
  output S, C;
  assign S = A ^ B;
  assign C = A & B;
endmodule
```


Arguments

Port Directions

assignments

Uppercase and lowercase letters
are distinguished

Port Directions

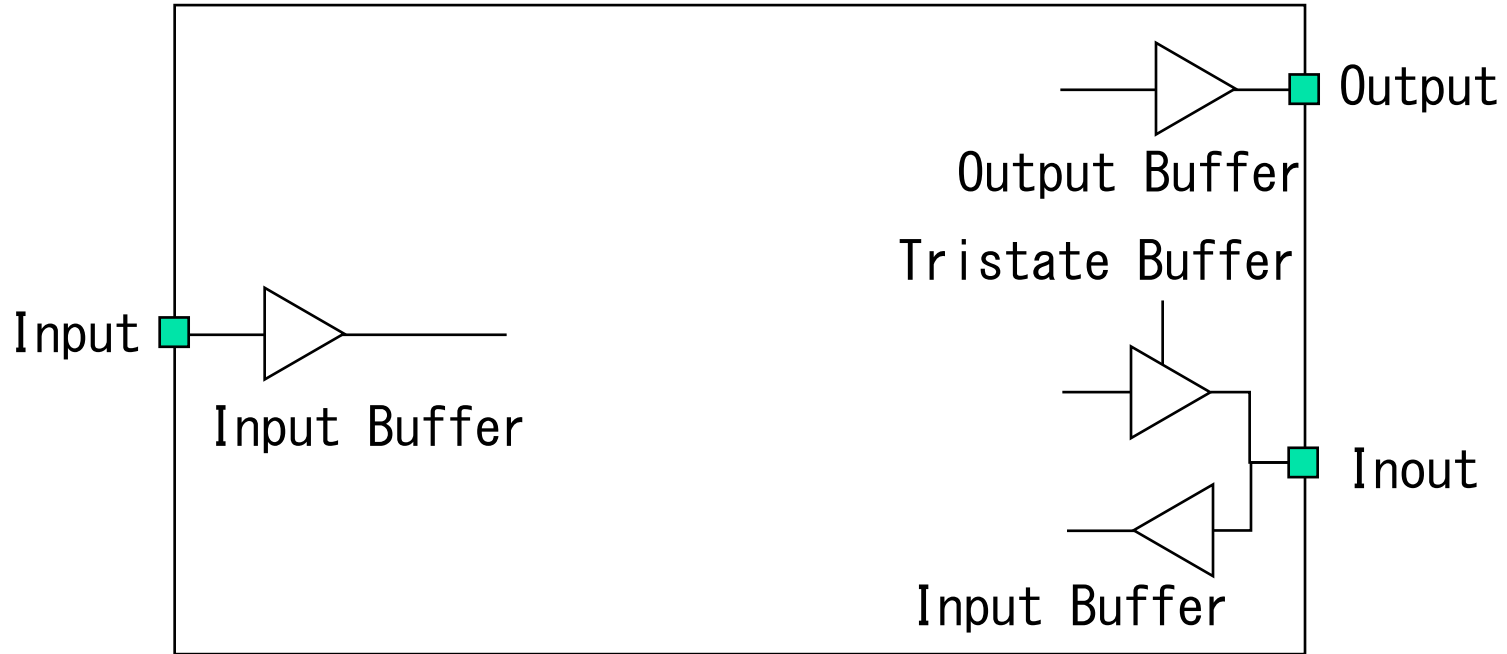

Don't need to describe I/O buffer instances in Verilog HDL because logic synthesizer can automatically insert adequate I/O buffers.

(You can explicitly insert I/O buffer instances.)




Values in Variable

- 4 types of signal value for digital simulation
 - '0' Low level
 - '1' High level
 - 'Z' High impedance
 - 'X' Unknown or Don't Care
- 8 strengths for transistor level simulation
 - supply Power line
 - strong Default signal strength
 - pull Pull-up signal
 - large
 - weak
 - medium
 - small
 - highz High impedance

Don't care "strengths"
in digital circuit design

Structured Description (Full Adder)①

 

Block Diagram of Full Adder

Variable type defined by input or output is "wire".

```
module fulladder ( A, B, Cin, S , Cout );
    input  A, B, Cin;
    output S, Cout;
```

"assign" statement is used for wire type.

```
// Internal wires
wire  Temp_S, Temp_C1, Temp_C2;
```

```
assign Cout = Temp_C2 | Temp_C1;
```


The order of arguments match in the lower layer and the upper layer as same as conventional programming languages.

```
halfadder hf1 ( A,      B,      Temp_S , Temp_C1 );
halfadder hf2 ( Temp_S, Cin,      S , Temp_C2 );
endmodule
```

Module name

Instance name (for identifying module)

Structured Description (Full Adder)②

 

Block Diagram of Full Adder

Variable type defined by input or output is "wire".

```
module fulladder ( A, B, Cin, S , Cout );
    input  A, B, Cin;
    output S, Cout;
```

"assign" statement is used for wire type.

```
// Internal wires
wire    Temp_S, Temp_C1, Temp_C2;

assign Cout = Temp_C2 | Temp_C1;
```

Dot notation can explicitly describe correspondence relationship of dummy and actual argument. (Recommend to this notation)

```
halfadder hf1 ( .A(A),      .B(B),      .S(Temp_S), .C(Temp_C1) );
halfadder hf2 ( .A(Temp_S), .B(Cin),   .S(S),      .C(Temp_C2) );
endmodule
```

Dummy argument
(Lower layer)


actual argument
(this layer)



Introduction to Verilog HDL


Combinational Logic Design with
abstracted (behavioral) description
than gate level

1-bit Adder (behavioral description)

 


```
module adder ( A, B, S, C )  
  input  A, B;  
  output C, S;  
  
  assign {C, S} = A + B;  
endmodule
```


'+' operator for addition

 

Logic synthesis

 


16-bit Adder

 


```
module adder ( A, B, S )  
  input  [15:0] A, B;  
  output [15:0] S;  
  
  assign S = A + B;  
endmodule
```

Bus type variable

'+' operator for addition

 


Logic synthesis

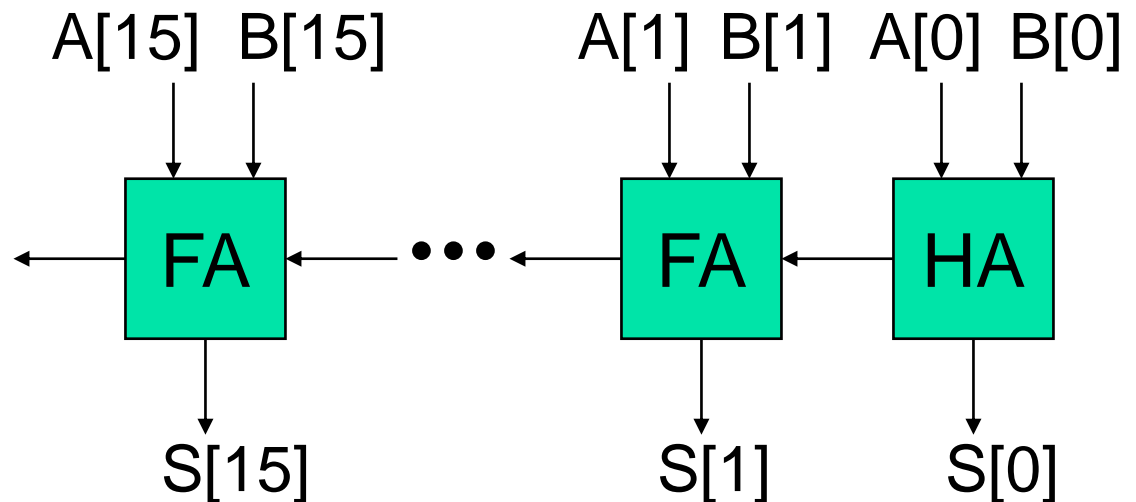

Adder algorithm is depend on constraints in logic synthesis.

16-bit Adder with Flags

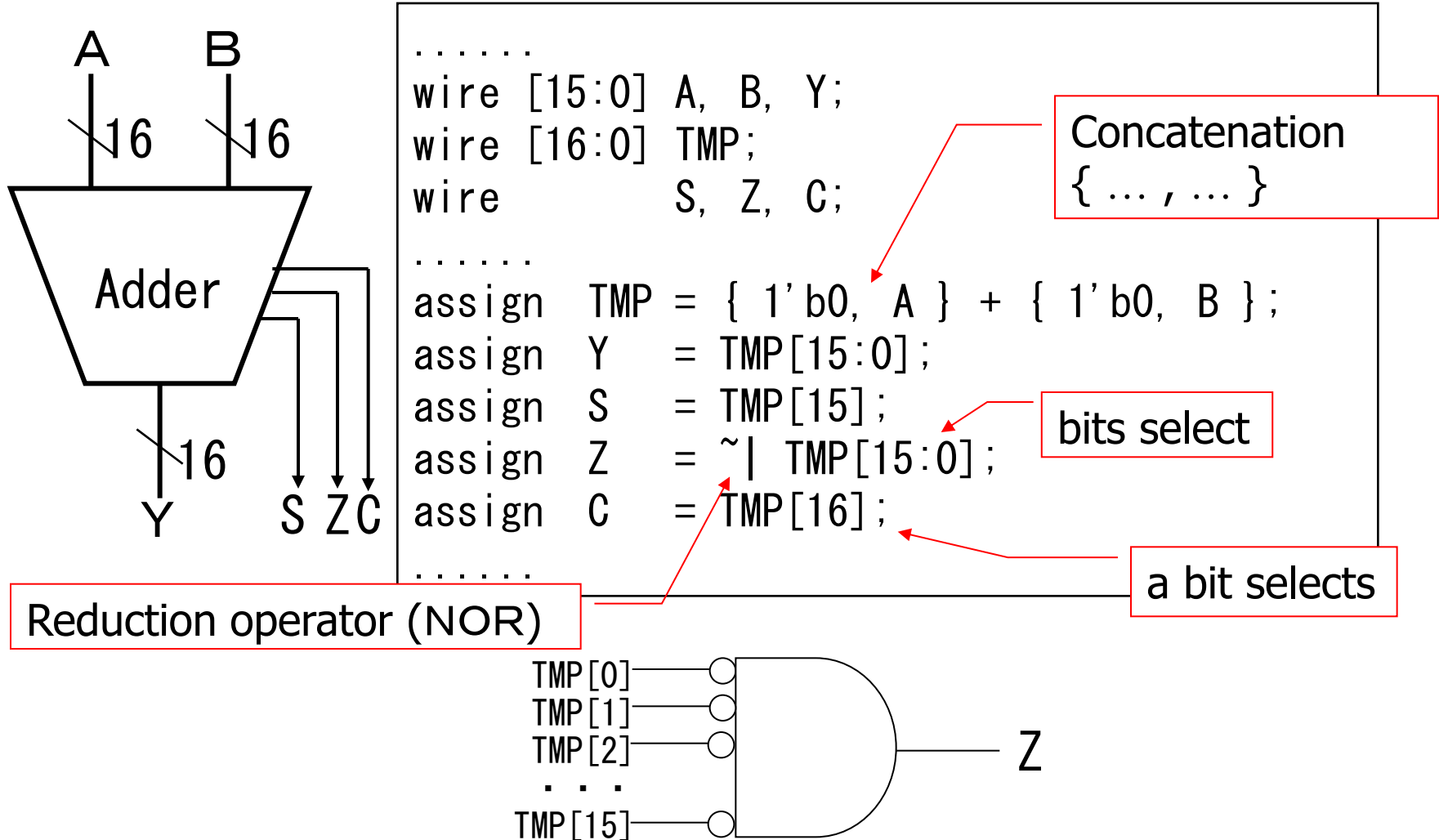Example of getting sign, carry and zero flags.



Constant Expression

■ Binary

- `8'b01010101` 8-bit binary "01010101"
- `8'b0101_0101` Use "_" for readability

■ Octal

- `6'o65` 6-bit binary "110101"

■ Decimal

- `4'd10` 4-bit binary "1010"
- `10` 32-bit binary "0...01010"

■ Hexadecimal

- `8'ha5` 8-bit binary "10100101"


Value

Radix(b, o, d, h)

Number of digits by binary

Bus Wire

 - Define 4 lines, such as A[3], A[2], A[1], A[0] by "wire [3:0] A"
- 4-bit Adder is described simply by "S = A + B"




```
.....  
wire [3:0] A, B, S;  
.....  
assign S = A + B;  
.....
```

Concatenation


a bit selects

multi bits select

 


Reduction Operation (wire [3:0] A)

- AND `assign Y=&A;`
- NAND `assign Y=~&A;`
- OR `assign Y=|A;`
- NOR `assign Y=~|A;`
- ExOR `assign Y=^A;`
- ExNOR `assign Y=~^A;`

 

2-to-1 Multiplexer

 



assign statement

```
.....
wire Y;
.....
assign Y = ( S == 0 ) ? A : B;
.....
```

Ternary operator
as same as C

"assign" statement is used
for wire type.

  When S has unknown value,
Y is assigned the value in B.
It differs from simulation result
and real behavior.



always statement

```
reg Y;
always @( A or B or S )
begin
    case( S )
        1'b0:    Y <= A;
        1'b1:    Y <= B;
        default: Y <= 1'bX;
    endcase
end
```




Assigned variable
must be "reg" type

In sensitivity list is
enumerated all
referenced variable
at always block

When S has unknown value,
Y is assigned unknown value 'X'.
It is effective for debugging.

"assign" statement is not
used for "reg" type variable

4-to-1 Multiplexer

   

```
reg Y;
always @( A or B or C or D or S )
begin
    case( S )
        2' b00:    Y <= A;
        2' b01:    Y <= B;
        2' b10:    Y <= C;
        2' b11:    Y <= D;
        default: Y <= 1' bX;
    endcase
end
```

Assigned variable must be "reg" type

In sensitivity list is enumerated all referenced variable at always block


When S has unknown value, Y is assigned unknown value 'X'. It is effective for debugging.

"assign" statement is not used for "reg" type variable

Decoder

■ 3-to-8 Decoder

 - A value '1' is assigned to only one output line in corresponding input value.



3-to-8 Decoder (case and if statements)

case statement

```
module decoder (din, dout);
    input  [2:0] din;
    output [7:0] dout;

    reg      [7:0] dout;

    always @( din )
    begin
        case ( din )
            3'b000: dout <=8' b0000_0001;
            3'b001: dout <=8' b0000_0010;
            3'b010: dout <=8' b0000_0100;
            3'b011: dout <=8' b0000_1000;
            3'b100: dout <=8' b0001_0000;
            3'b101: dout <=8' b0010_0000;
            3'b110: dout <=8' b0100_0000;
            3'b111: dout <=8' b1000_0000;
            default:dout <=8' bXXXX_XXXX;
        endcase
    end
endmodule
```

Assigned variable must be "reg" type in "always" block.

if statement

```
module decoder (din, dout);
    input  [2:0] din;
    output [7:0] dout;

    reg      [7:0] dout;

    always @( din )
    begin
        if (dout==3' b000) dout<=8' b0000_0001;else
        if (dout==3' b001) dout<=8' b0000_0010;else
        if (dout==3' b010) dout<=8' b0000_0100;else
        if (dout==3' b011) dout<=8' b0000_1000;else
        if (dout==3' b100) dout<=8' b0001_0000;else
        if (dout==3' b101) dout<=8' b0010_0000;else
        if (dout==3' b110) dout<=8' b0100_0000;else
        if (dout==3' b111) dout<=8' b1000_0000;else
            dout<=8' bXXXX_XXXX;
    end
endmodule
```


Assigned variable must be "reg" type

In sensitivity list is enumerated all referenced variable at always block

When "din" has unknown value, "dout" is assigned unknown value "X".
It is effective for debugging.

7-segment Decoder

- 7-segment decoder

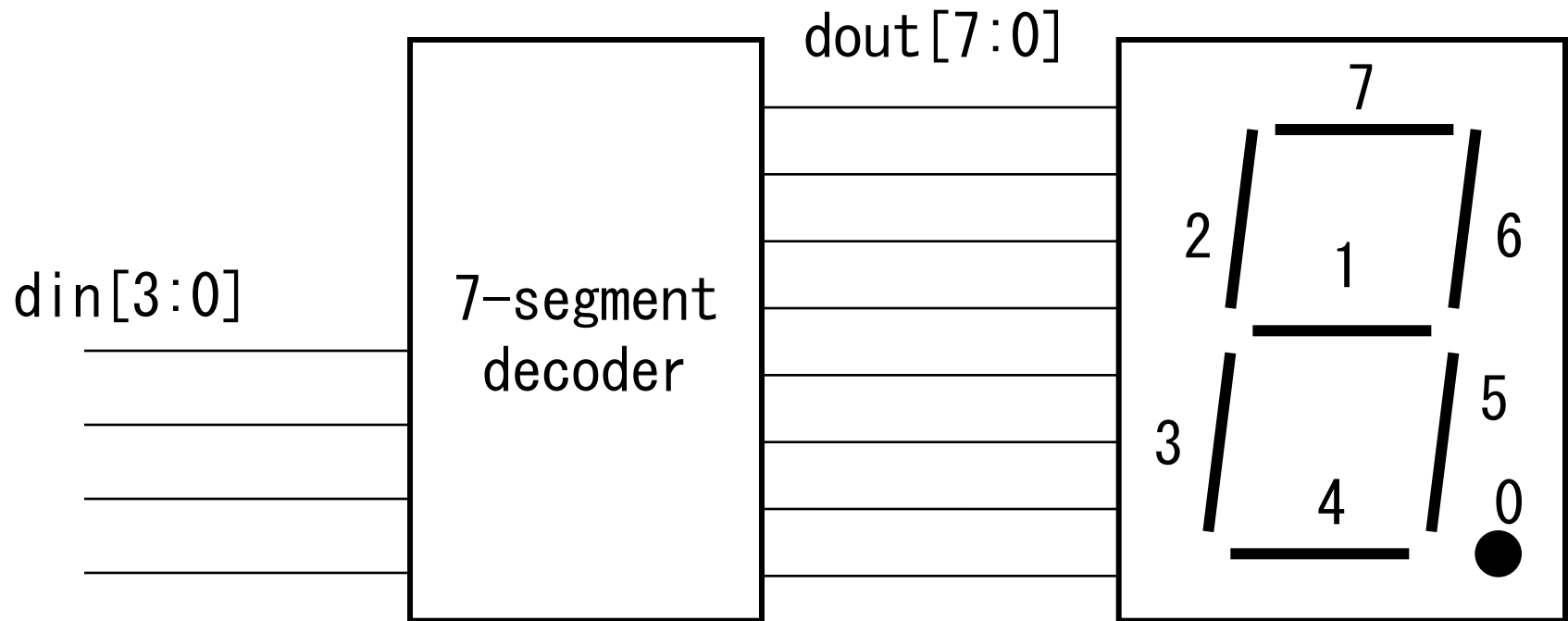

7-segment Decoder

```
module seven_seg(din, dout);  
  input  [3:0] din;  
  output [7:0] dout;  
  
  reg    [7:0] dout;  
  
  always @( din )  
  begin  
    case ( din )  
      4' b0000:dout<=8' b11111100;  
      4' b0001:dout<=8' b01100000;  
      .....  
      .....  
      4' b1110:dout<=8' b10011110;  
      4' b1111:dout<=8' b10001110;  
      default:dout<=8' bXXXXXXXX;  
    endcase  
  end  
endmodule
```

Assigned variable must be "reg" type in "always" block.


In sensitivity list is enumerated all referenced variable at always block

Assigned variable must be "reg" type in "always" block. Int

When "din" have unknown value, "dout" is assigned unknown value "X". It is effective for debugging.

Priority Encoder

- Decimal to binary priority encoder

 

When the one of ten inputs "din" from 0 to 9 is "1", corresponding binary value is output to the "dout".
Also a valid binary value to "dout" is output, "en" becomes "1".

Priority Encoder

You should use "case~~ex~~" statement to make a prioritized circuit.


```
module priority_encoder (din, dout, en);
    input  [9:0] din;
    output [3:0] dout;
    output          en;
    reg  [3:0] dout;
    reg          en;
    always @( din )
    begin
        caseex ( din )
            10'b?????_????1: { en, dout } <=5'b1_0000;
            10'b?????_????10: { en, dout } <=5'b1_0001;
            10'b?????_??100: { en, dout } <=5'b1_0010;
            10'b?????_?1000: { en, dout } <=5'b1_0011;
            10'b?????_10000: { en, dout } <=5'b1_0100;
            10'b????1_00000: { en, dout } <=5'b1_0101;
            10'b???10_00000: { en, dout } <=5'b1_0110;
            10'b??100_00000: { en, dout } <=5'b1_0111;
            10'b?1000_00000: { en, dout } <=5'b1_1000;
            10'b10000_00000: { en, dout } <=5'b1_1001;
            default:         { en, dout } <=5'b0_XXXX;
        endcase
    end
endmodule
```

Assigned variable must be "reg" type in "always" block.

In sensitivity list is enumerated all referenced variable at always block

3-to-1 Multiplexer ①

■ Correctness ①

 




$Y \leq 0$ when $S == 2'b11$

```
reg Y;
always @( A or B or C or S )
begin
  case( S )
    2'b00:   Y <= A;
    2'b01:   Y <= B;
    2'b10:   Y <= C;
    default: Y <= 1'b0;
  endcase
end
```

In this case, synthesized logic circuit is in the left side figure.

3-to-1 Multiplexer ②

■ Correctness ②

   

Don't care

```
reg Y;  
always @( A or B or C or S )  
begin  
    case( S )  
        2'b00:    Y <= A;  
        2'b01:    Y <= B;  
        2'b10:    Y <= C;  
        default:  Y <= 1'bX;  
    endcase  
end
```

"Y" becomes X, when
"S=2'b11" by default.




default

```
reg Y;  
always @( A or B or C or S )  
begin  
    case( S )  
        2'b00:    Y <= A;  
        2'b01:    Y <= B;  
        default:  Y <= C;  
    endcase  
end
```

"Y" becomes C, when
"S=2'b1X" by default.

3-to-1 Multiplexer ③

■ Correctness ③

 
 
 


case statement

```
reg Y;  
always @( A or B or C or S )  
begin  
    case( S )  
        2'b00:    Y <= A;  
        2'b01:    Y <= B;  
        2'b1?:    Y <= C;  
        default: Y <= 1'bX;  
    endcase  
end
```

S[0] is treated as "Don't Care" by 2'b1?. Also "Y" becomes X, when "Y<=1'bX" by default.

3-to-1 Multiplexer ④

   


Mis-description

```
reg Y;
always @( A or B or C or S )
begin
    case( S )
        2'b00: Y <= A;
        2'b01: Y <= B;
        2'b10: Y <= C;
        // 2'b11: Y <= D; // This line is missing
    endcase
end
```


without default

Transparent latch is synthesized because of holding a just before value when S becomes 2'b11.

Expected circuit

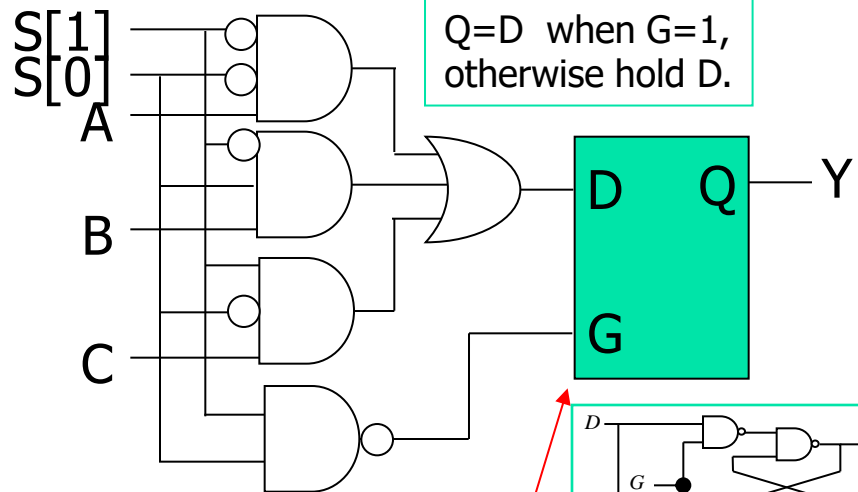

Transparent Latch

 


Synthesized circuit from mis-description

Fallible Description (inter always assignment)

Error

```
reg Y;  
  
always @( ... )  
begin  
    Y <= ...;  
end  
  
always @( ... )  
begin  
    Y <= ...;  
end
```

 Assign to same
Y from multiple
always blocks




It makes short circuit.
It is correct in syntax and can be simulated.
However, this description is not synthesizable.

Correctness

```
wire YA, YB;  
reg Y1, Y2;  
  
always @( ... )  
begin  
    Y1 <= ...;  
end  
  
always @( ... )  
begin  
    Y2 <= ...;  
end
```

- (1) Assign to differ variable (YA, YB) in always block, and select either one by assignment condition.
- (2) Inclusive OR is acceptable if no problem its behavior.

```
assign YA = ( 代入条件 ) ? Y1 : Y2;  
assign YB = Y1 | Y2;
```


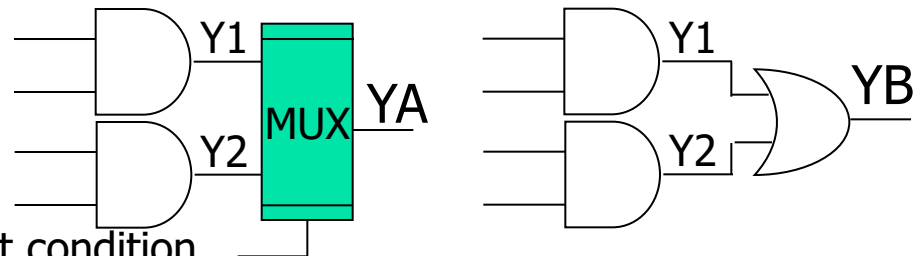




Introduction to Verilog HDL

Flip-Flop
Register
Counter

D-Flip Flop (1)

 
 


```
module dff ( D, Q, CLK );  
    input  D;  
    input  CLK;  
    output Q;  
  
    reg    tmp; // for Register  
  
    always @( posedge CLK )  
        begin  
            tmp <= D;  
        end  
  
    assign Q = tmp;  
  
endmodule
```

Positive edge,
"negedge" for
negative edge

"D" is assigned to "tmp" when positive edge clock,
otherwise "tmp" never changes.



D-Flip Flop (2)

  

```
module dff ( D, Q, CLK );  
    input  D;  
    input  CLK;  
    output Q;  
  
    reg    Q;  
  
    always @( posedge CLK )  
        begin  
            Q <= D;  
        end  
  
endmodule
```

"D" is assigned to "Q" when positive edge clock, otherwise "Q" never changes.

D-Flip Flop with Asynchronous Reset

 
 


```
module dff ( D, Q, CLK, RST );  
    input D, CLK, RST;  
    output Q;  
  
    reg    tmp; // for Register  
  
    always @(posedge RST or posedge CLK)  
    begin  
        if ( RST ) tmp <= 1'b0; else  
            tmp <= D;  
        end  
  
    assign Q = tmp;  
  
endmodule
```

Reset condition

"0" is assigned to "tmp" when RST is active, else "D" assigned to "tmp" when positive edge clock, otherwise "tmp" never changes.

D-Flip Flop with Synchronous Reset

  



```
module dff ( D, Q, CLK, RST );  
    input D, CLK, RST;  
    output Q;  
  
    reg    tmp; // for Register  
  
    always @( posedge CLK )  
    begin  
        if ( RST ) tmp <= 0; else  
            tmp <= D;  
    end  
  
    assign Q = tmp;  
  
endmodule
```

When Reset

"0" is assigned to "tmp" when positive edge clock and active RST, else "D" assigned to "tmp" when positive edge clock, otherwise "tmp" never changes.

D-Flip Flop with Write Enable

  WE: Write Enable WE
same as CE (Clock Enable)



D is held in Q when active
WE and positive edge clock.

```
module dff_we ( D, WE, Q, CLK );
```

```
    input  D;
```

```
    input  WE;
```

```
    input  CLK;
```

```
    output Q;
```

Don't include WE to
sensitivity list

```
    reg    tmp;
```

```
    always @( posedge CLK )
```

```
    begin
```


```
        if( WE ) tmp <= D;
```

```
    end
```



```
    assign Q = tmp;
```

```
endmodule
```

D-Flip Flop with Write Enable

 

 
 
D is held in Q when active WE and positive edge clock.



Generally, gated clock circuit is not used in synchronous circuit design, although it used aggressive low-power consumption circuit design.

8-bit Register

  WE: Write Enable WE
same as CE (Clock Enable)



D is held in Q when active
WE and positive edge clock.



8-bit Register

8-bit register with asynchronous reset

```
module reg8_ar ( D, WE, RST, Q, CLK );
  input  [7:0] D;
  input          WE;
  input          RST;
  input          CLK;
  output [7:0] Q;

  reg  [7:0] tmp;

  always @(posedge RST or posedge CLK)
  begin
    if ( RST ) tmp <= 8'h00; else
    if ( WE ) tmp <= D;
  end

  assign Q = tmp;
endmodule
```

8-bit register with synchronous reset

```
module reg8_sr ( D, WE, RST, Q, CLK );
  input  [7:0] D;
  input          WE;
  input          RST;
  input          CLK;
  output [7:0] Q;

  reg  [7:0] tmp;


  always @(posedge CLK)
  begin
    if( RST ) tmp<=8'h00; else
    if( WE ) tmp<=D;
  end

  assign Q = tmp;
endmodule
```


D is held in Q when active WE and positive edge clock.

Schematic of 8-bit Register


8-bit register with asynchronous reset

 

Pre-settable 4-bit Binary Counter (1)

 

Recommended this style

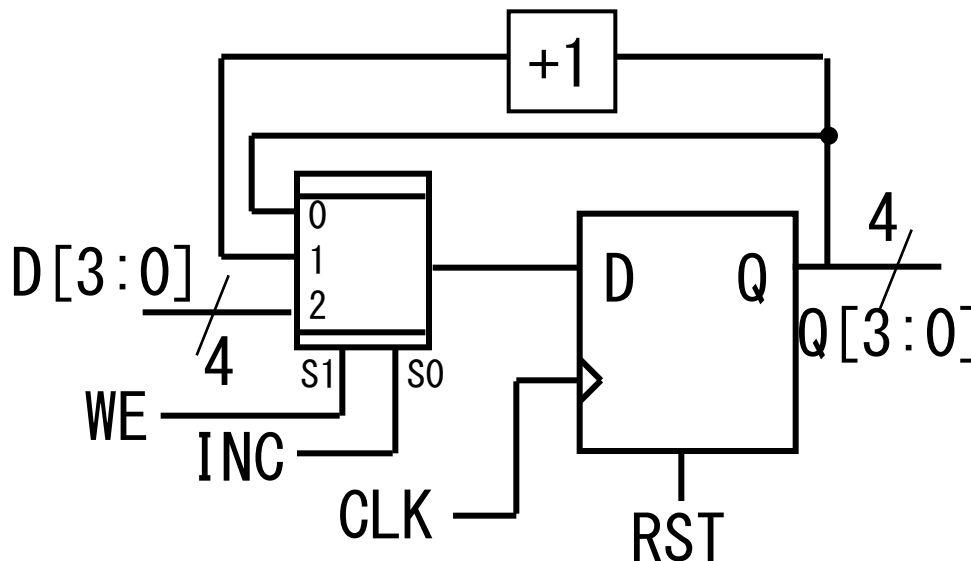


```
module count4 ( D, WE, INC, RST, Q, CLK );
    input  [3:0] D;
    input      WE;
    input      INC;
    input      RST;
    input      CLK;
    output [3:0] Q;

    reg  [3:0] tmp; // for Register

    always @(posedge RST or posedge CLK)
    begin
        if ( RST == 1 ) tmp <= 4'h0; else
        if ( WE == 1 ) tmp <= D;      else
        if ( INC == 1 ) tmp <= tmp + 1;
    end
    assign Q = tmp;
endmodule
```

Block diagram


Pre-settable 4-bit Binary Counter (2)

 

Write Enable

Increment

Symbol

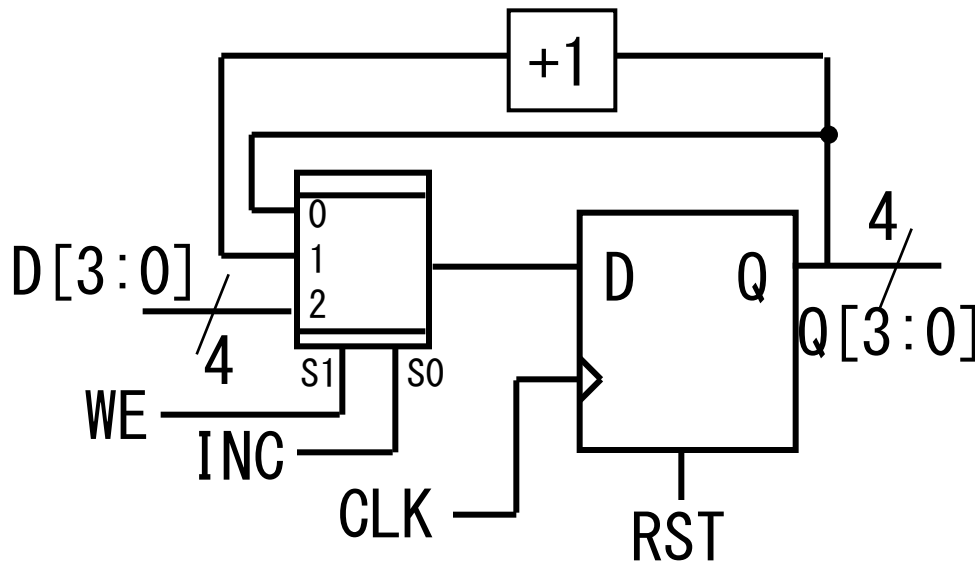

Block diagram

Not recommended this style

```
module count4 ( D, WE, INC, RST, Q, CLK );  
    input  [3:0] D;  
    input      WE;  
    input      INC;  
    input      RST;  
    input      CLK;  
    output [3:0] Q;  
  
    reg  [3:0] Q; // for Register  
  
    always @(posedge RST or posedge CLK)  
    begin  
        if ( RST == 1 ) Q <= 4'h0; else  
        if ( WE == 1 ) Q <= D;      else  
        if ( INC == 1 ) Q <= Q + 1;  
    end  
  
endmodule
```



Non-blocking and Blocking assignment

- Non-blocking assignment
 - Use "<=" sign
 - Assignment don't take place immediately
 - Assignment takes place after a Δ delay
 - Δ delay: infinitesimal time for accuracy simulation
- Blocking assignment
 - Use "=" sign
 - Assignment takes place immediately w/o Δ delay
 - Following assignment can read the previous assignment.

Note that non-blocking and blocking assignments cannot be mixed in one always statement.

Ring Counter

Non-blocking assignment


```
module nonblocking ( CLK, RST, Q );  
    input          CLK, RST;  
    output [2:0] Q;  
  
    reg [2:0] tmp;  
  
    always @( posedge CLK or posedge RST)  
    begin  
        if( RST ) tmp <= 3'b001;  
        else  
            begin  
                tmp[1] <= tmp[0];  
                tmp[2] <= tmp[1];  
                tmp[0] <= tmp[2];  
            end  
        end  
  
        assign Q = tmp;  
    endmodule
```

Blocking assignment

```
module blocking ( CLK, RST, Q );  
    input          CLK, RST;  
    output [2:0] Q;  
  
    reg [2:0] tmp;  
  
    always @( posedge CLK or posedge RST)  
    begin  
        if( RST ) tmp = 3'b001;  
        else  
            begin  
                tmp[1] = tmp[0];  
                tmp[2] = tmp[1];  
                tmp[0] = tmp[2];  
            end  
        end  
  
        assign Q = tmp;  
    endmodule
```

- Ring counter is correctly synthesized by non-blocking assignment.
- Assignments are taken place simultaneously at the end of always block.
- In blocking assignment, tmp[0] value is immediately assigned to tmp[1] and tmp[2]. In this result, the synthesized circuit can't behave as a ring counter.
- Non-blocking assignment is recommended in "always block" to prevent a mistaking design.
- Note the use of blocking assignment although there are effective cases.

Schematic of Ring Counter

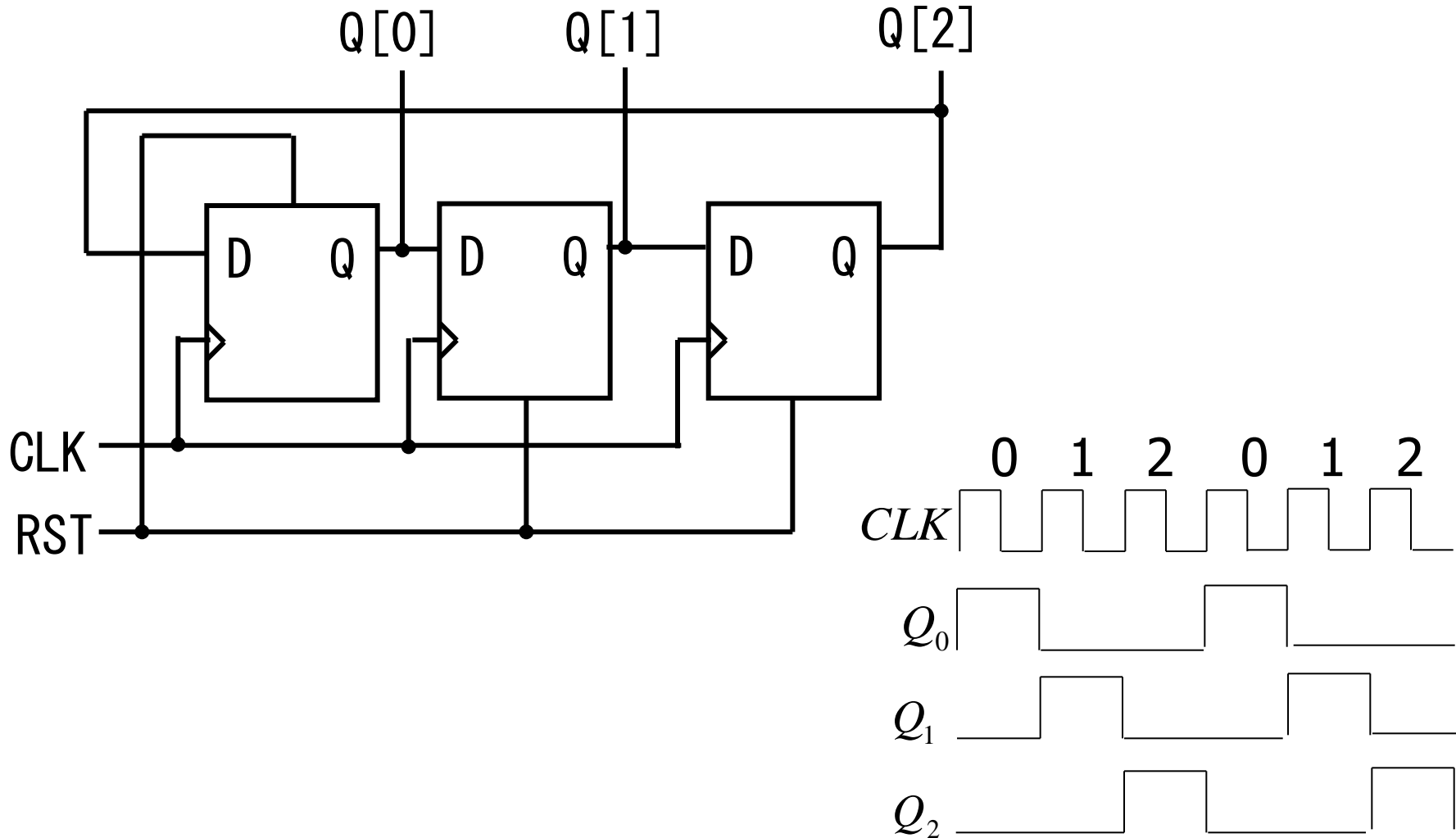

BCD Adder

Non-blocking assignment


```
module bcd_addr ( A, B, S, C );  
  input  [3:0] A, B;  
  output [3:0] S;  
  output          C; // Carry  
  reg  [4:0] tmp;  
  always @( A or B )  
  begin  
    tmp <= { 1'b0, A } + { 1'b0, B };  
    if( tmp >= 5'b01010 )  
      tmp <= tmp + 5'b00110;  
  end  
  assign S = tmp[3:0];  
  assign C = tmp[4];  
endmodule
```

Blocking assignment

```
module bcd_addr ( A, B, S, C );  
  input  [3:0] A, B;  
  output [3:0] S;  
  output          C; // Carry  
  reg  [4:0] tmp;  
  always @( A or B )  
  begin  
    tmp = { 1'b0, A } + { 1'b0, B };  
    if( tmp >= 5'b01010 )  
      tmp = tmp + 5'b00110;  
  end  
  assign S = tmp[3:0];  
  assign C = tmp[4];  
endmodule
```

- BCD adder is correctly synthesized by blocking assignment.
- In blocking assignment, tmp value is immediately assigned. You can see properly immediately after.
- In non-blocking assignment, not correctly behaves because assignments are taken place simultaneously at the end of always block.
- This case is only described by blocking assignment.

Block Diagram of BCD Adder

 

Block diagram

BCD adder adds 2 values of binary coded decimal number. First, A and B are added by binary adder. If the result is from 0 to 9, it is correct. However, when the result is $(A)_{16} \sim (F)_{16}$, the result has to be correction so that the result becomes to BCD value. For correction, constant 6 adds to the result. For example, the result is $(A)_{16}$ when A adds B, then the result of adding 6 is $(10)_{16}$ or $(10)_{10}$ of BCD.

Similarly, when the result is $(F)_{16}$, then the result of adding 6 is $(15)_{16}$ or $(15)_{10}$ of BCD.

Pipelined BCD Adder

```


module bcd_pipe_addr ( CLK, A, B, S, C );
    input      CLK;
    input  [3:0] A, B;
    output [3:0] S;
    output      C; // Carry
    reg  [4:0] tmp1, tmp2;

    always @( posedge CLK )
    begin
        tmp1 <= { 1'b0, A } + { 1'b0, B };
        if( tmp1 >= 5'b01010 )
            tmp2 <= tmp1 + 5'b00110;
        else
            tmp2 <= tmp1;
    end

    assign S = tmp2[3:0];
    assign C = tmp2[4];
endmodule

```

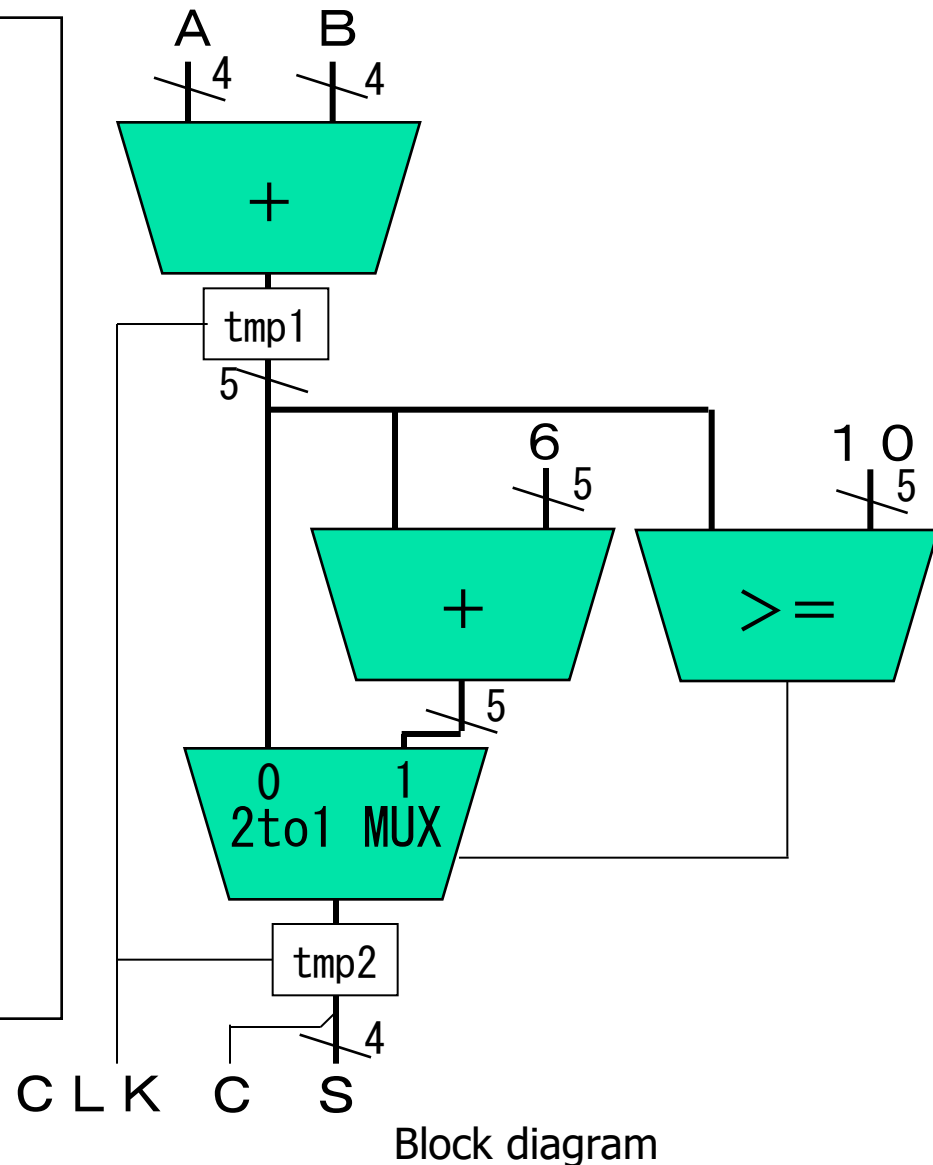Pipelined BCD adder is described by blocking assignment.





Introduction to Verilog HDL


Tristate Buffer and Bidirectional Input/Output

Why Need Tristate Buffer?

Should not connect typical output pins.




 Right figure shows short circuit.
Transistors are destroyed
because of over current.



How do we describe bi-directional
line or bus line?


Tristate buffer

 

Tristate Buffer

機能表

OE	Y
0	Z
1	A

 

always statement can be described at complex output condition.

```

reg [15:0] Y;
always @( tmp or OEH or OEL )
begin
    if ( OEH == 1 )      Y <= { tmp[15:8], 8'hZZ };
    else if ( OEL == 1 ) Y <= { 8'hZZ, tmp[7:0] };
    else                 Y <= 16'hZZZZ;
end
    
```

How to use the Tristate Buffer

Tristate Buffer utilized for bidirectional buffer.




The one time, only one device can output a value.

All devices can be read the value on the bus line.

```
module dev1 ( DATA );
  inout  [15:0] DATA;

  wire [15:0] DATAI, DATAO;
  wire      OE;

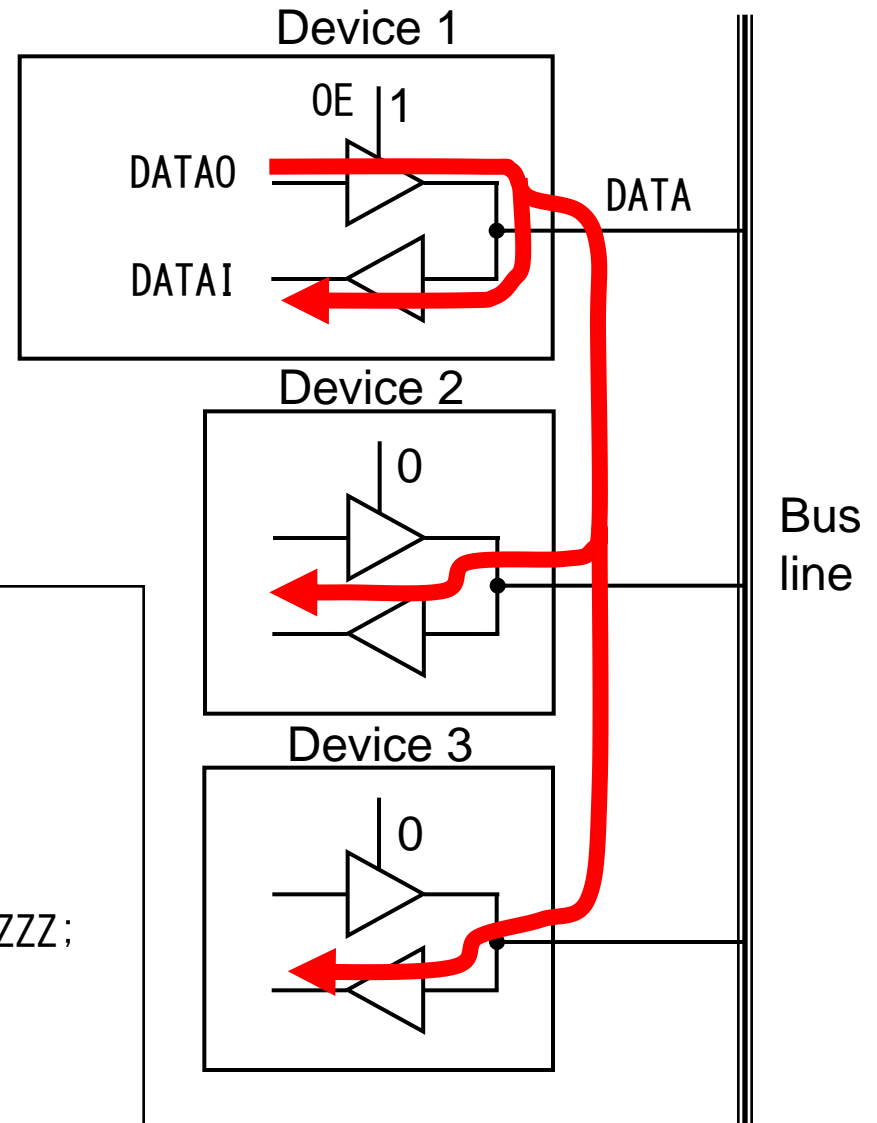  assign DATA = ( OE ) ? DATAO : 16'hZZZZ;
  ...
  assign DATAI = DATA;
  ...
endmodule
```








Introduction to Verilog HDL

Sequential logic

Sequential Logic

  

Wave form

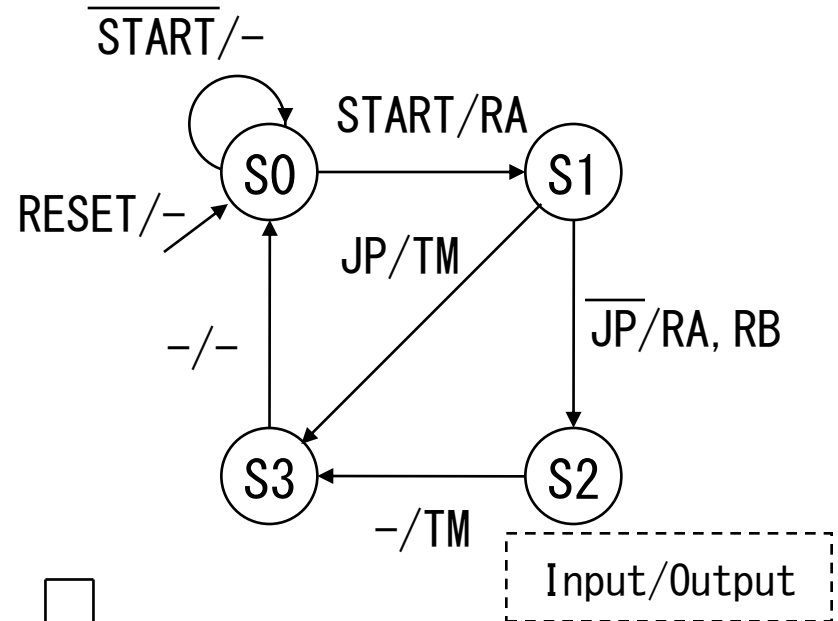

State transition diagram

Sequencer (State machine)

```

`define S0 2'b00 // define states
`define S1 2'b01
`define S2 2'b10
`define S3 2'b11

```

```

module sequencer ( START, JP, RESET, CLK, RA, RB, TM );
  input  START, JP, RESET, CLK;
  output RA, RB, TM;

```

```

  reg  RA, RB, TM;
  reg  [1:0] STATE; // state variable

```

```

  // state machine
  always @( posedge RESET or posedge CLK )
  begin
    if( RESET == 1 ) // asynchronous reset
      STATE <= `S0;

```

```


  else
    case ( STATE )
      `S0 : if( START == 1 ) STATE <= `S1; // transition start
      `S1 : if( JP == 1 ) STATE <= `S3; // jump
            else STATE <= `S2;
      `S2 : STATE <= `S3;
      `S3 : STATE <= `S0; // become initial state
    endcase

```

```

end

```

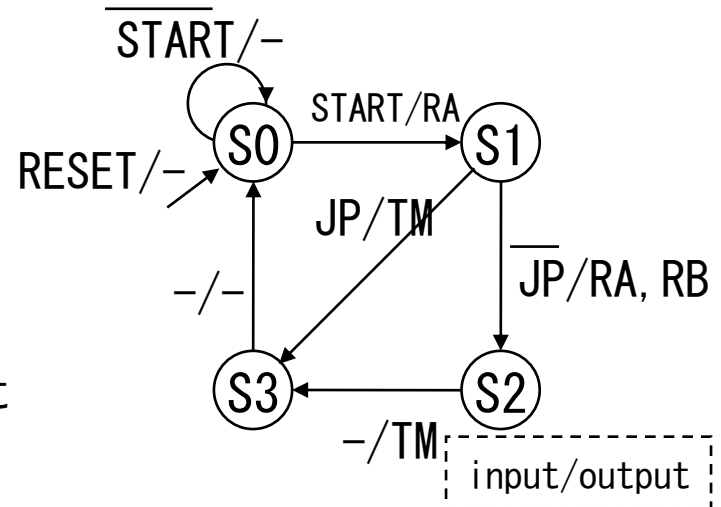

Sequencer (Generate control signals)

Case 1

```
// control signals
always @( STATE )
begin
  case ( STATE )
    `S0 : begin RA <= 0; RB <= 0; TM <= 0; end
    `S1 : begin RA <= 1; RB <= 0; TM <= 0; end
    `S2 : begin RA <= 1; RB <= 1; TM <= 0; end
    `S3 : begin RA <= 0; RB <= 0; TM <= 1; end
    default : begin RA <= 0; RB <= 0; TM <= 0; end
  endcase
end
endmodule
```

Should assign a value to all variables in all cases, or logic synthesizer makes unexpected transparent latches.

Case 2

```
// control signals
always @( STATE )
begin
  RA <= 0;
  RB <= 0;
  TM <= 0;
  case ( STATE )
    `S1 : begin RA <= 1; end
    `S2 : begin RA <= 1; RB <= 1; end
    `S3 : begin TM <= 1; end
  endcase
end
endmodule
```

default value

assign '1' if necessary

Operators in Verilog HDL

Binary arithmetic

·Addition	+
·Subtraction	—
·Multiply	*
·Divide	/
·Modulo	%

Unary arithmetic

·Plus	+
·Minus	—

Relational

·Equal	==
·Not equal	!=
·Less	<
·Greater	>
·Less than	<=
·Greater than	>=
·Not	!
·And	&&
·Or	

Binary logical

·And	&
·Or	
·Exclusive Or	^

Unary logical

·Complement	~
-------------	---

Reduction

·And	&
·Nand	~&
·Or	
·Nor	~
·Exclusive Or	^
·Exclusive Nor	^^

Bit operation

·Concatenation	{ ... , ... }
----------------	---------------